

# **Average Power in AC Circuits**

**05.06.09**

**By Amarbir  
Singh**

**(M.Sc. Physics, M.Ed.)**

**Edusat Society, Punjab**

## **Average Power in AC circuits**

Let the instantaneous voltage be  $E = E_0 \sin \omega t$  (or  $E_0 \cos \omega t$ ). The resulting current is left out of phase say by an angle  $\phi$ , with voltage and as such is given by  $I = I_0 \sin (\omega t - \phi)$

The instantaneous power  $P$  hence is given by

$$\begin{aligned} P &= V.I = E_0 \sin \omega t. I_0 \sin (\omega t - \phi) \\ &= E_0 I_0 \sin \omega t (\sin \omega t \cos \phi - \\ &\hspace{15em} \sin \phi \cos \omega t) \end{aligned}$$

# **Average Power in AC circuits**

$$= E_0 I_0 (\sin 2\omega t \cdot \cos \phi - \sin \omega t \cdot \cos \omega t \sin \phi)$$

$$\text{Or } P = E_0 I_0 (\sin 2\omega t \cdot \cos \phi - (1/2) 2 \sin \omega t \cdot \cos \omega t \sin \phi)$$

$$= E_0 I_0 [\sin 2\omega t \cdot \cos \phi - (1/2) \sin 2\omega t \cdot \sin \phi]$$

# **Average Power in AC circuits**

**But in A.C. circuits we take Average Power over a complete cycle, Average power therefore is total energy consumed in one cycle, divided by the time period  $T$  of the cycle i.e. average power**

# Average Power in AC circuits

$$P_{av} = \frac{\int_0^T P \cdot dt}{\int_0^T dt} = \frac{\int_0^T P \cdot dt}{[T - 0]} = \frac{1}{T} \int_0^T P dt$$

$$= \frac{E_0 I_0}{T} \int_0^T \sin^2 \omega t \cos \phi dt - \frac{1}{2} \int_0^T \sin 2\omega t \cdot \sin \phi dt$$

# Average Power in AC circuits

$$= \frac{E_0 I_0}{T} \int_0^T \cos \phi \sin^2 \omega t \, dt - \frac{1}{2} \sin \phi \int_0^T \sin 2\omega t \, dt$$

$$\text{Now } \int_0^T \sin^2 \omega t \, dt = \int_0^T \frac{1 - \cos 2\omega t}{2} \, dt = \frac{t}{2} - \frac{\sin 2\omega t}{4\omega}$$

$$= \frac{E_0 I_0}{T} \left[ \frac{\sin 2\omega t}{4\omega} \right]_0^T - \frac{\sin 2\omega t}{4\omega} \Big|_0^T = \frac{E_0 I_0}{T} \left[ \frac{\sin 2\omega T}{4\omega} - \frac{\sin 0}{4\omega} \right] - \left[ \frac{\sin 2\omega T}{4\omega} - \frac{\sin 0}{4\omega} \right]$$

# Average Power in AC circuits

$$\begin{aligned}
 \text{and } \int_0^T \sin 2\omega t dt &= \left| -\cos \frac{2\omega t}{2\omega} \right|_0^T \\
 &= \frac{-\cos 2 \frac{2\pi}{T} \cdot T}{2\omega} - \frac{-\cos 2 \cdot \frac{2\pi}{T} \cdot 0}{2\omega} = \frac{1}{2\omega} - \frac{1}{2\omega} = 0
 \end{aligned}$$

$$P_{av} = \frac{E_0 I_0}{T} \left[ \cos \phi \cdot \frac{T}{2} - \frac{1}{2} \sin \phi \cdot 0 \right]$$

# **Average Power in AC circuits**

$$\text{Hence } P_{av} = \frac{E_0 I_0}{2} C \cos \phi = \frac{E_0 I_0}{\sqrt{2} \sqrt{2}} C \cos \phi$$

$$P_{av} = E_v I_v C \cos \phi$$

$C \cos \phi$  is called power factor

# Power Factor.

- **Here  $\cos \phi$  is called power factor**:- When we have a **pure resistance** in the circuit, the voltage and current are in the same phase i.e.  $\phi = 0^\circ$  and  $\text{Cos } \phi = 1$ . Equation (3) hence becomes.
- $P_{av} = E_{\text{eff}} \cdot I_{\text{eff}}$
- For a pure capacitor or pure inductor in an a.c. circuit,  $\phi = \pm 90^\circ$  and  $\text{Cos } \phi = 0$ .
- i.e. they do not consume any power. Hence are called wattless devices.

# Weightage of the topics covered

1. Electrostatics	-8
2. Current Electricity	-7
3. Magnetic Effects and Magnetism	-8
4. EMI and AC	-8
Total	-31

44% of the total syllabus has been covered.